

Integrated Circuit Design

Homework #1




Layout Reading

Deadline: Sep. 27

For the following layouts, please

- Draw the associated sticky diagram.
- Draw the circuit in transistor level.
- Describe the function of the circuits. (You can use Boolean equations or other descriptions)


1.

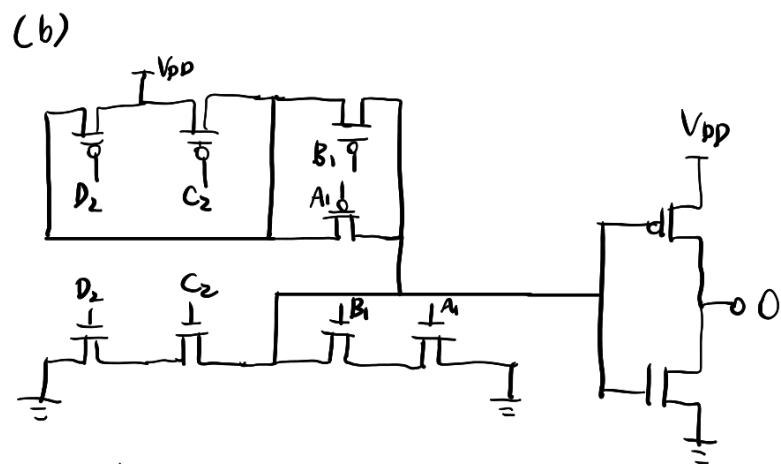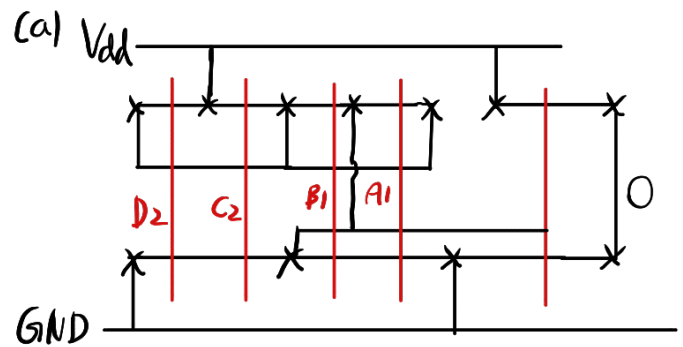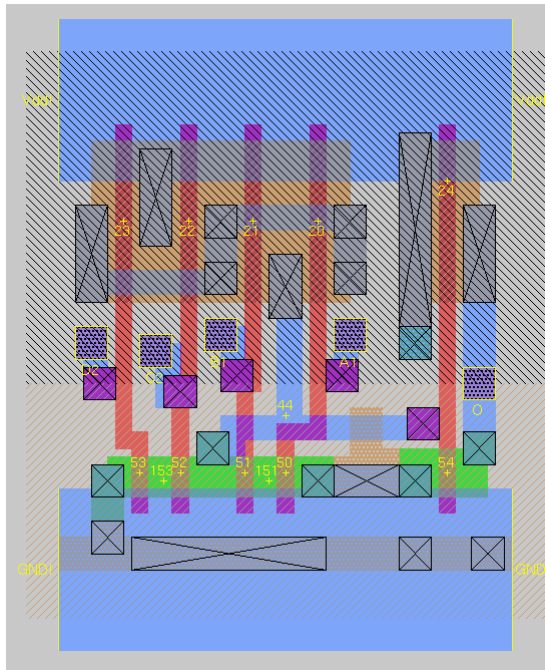


(c) Boolean equation for the output O :

$$O = A_1 B_1 + C_2 D_2$$


2.

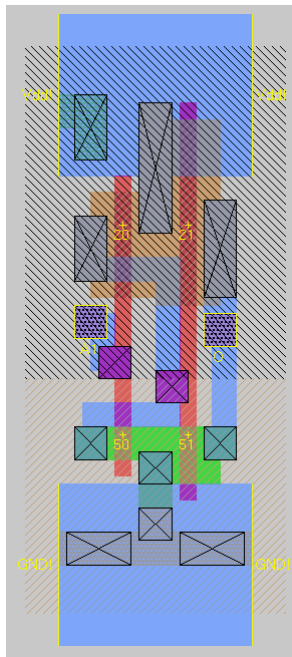

(a)

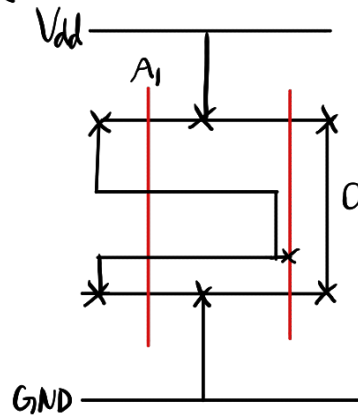


(b)

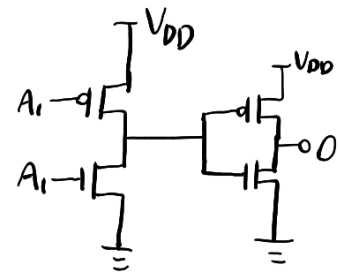


(c)

$$O = A_1$$


3.

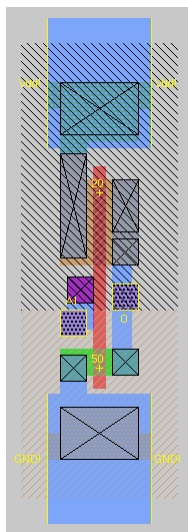

(a)

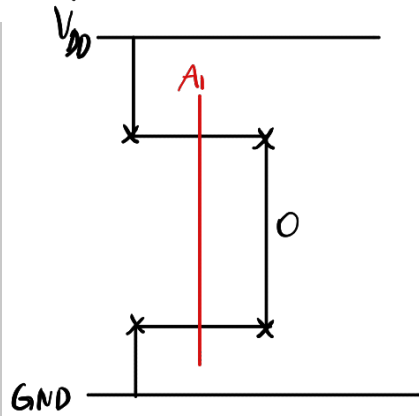




(b)

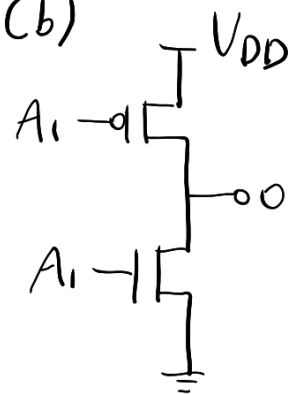

(c)




$$O = A_1'$$

4.

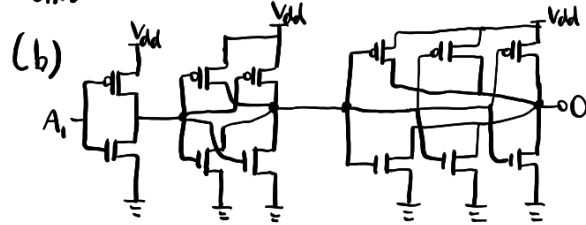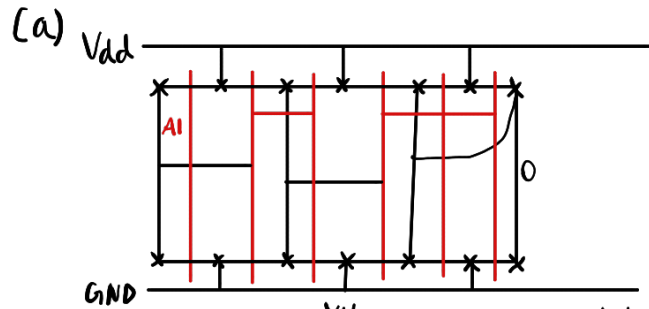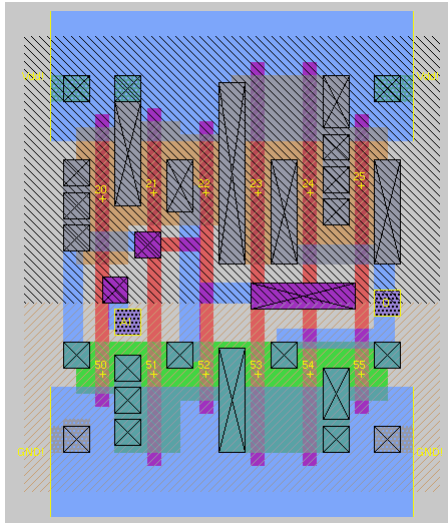




(c) $O = A_1'$

5.

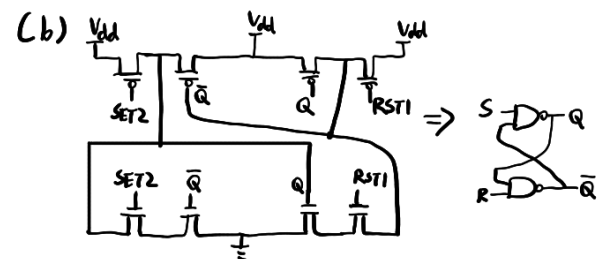
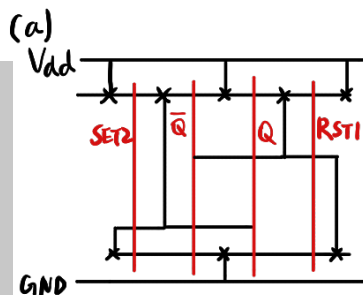
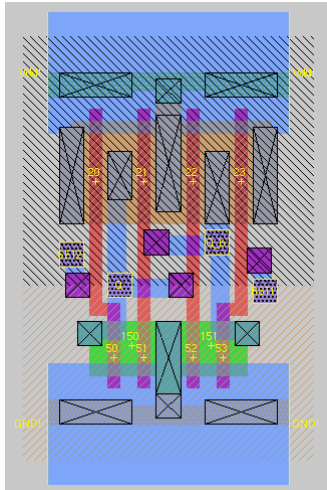


(c) $Q^+ = SET2' + RST1 \cdot Q$

6. Select

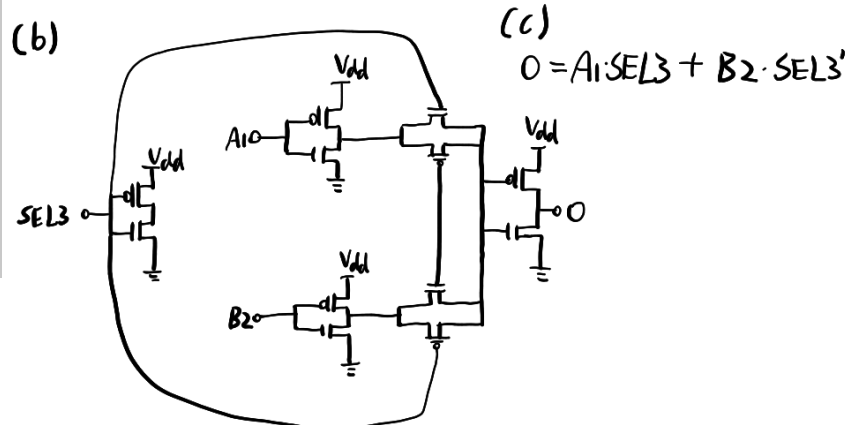
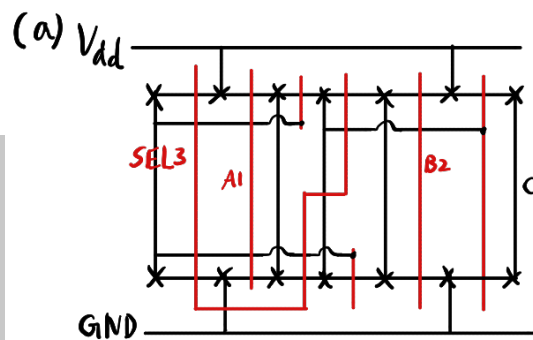
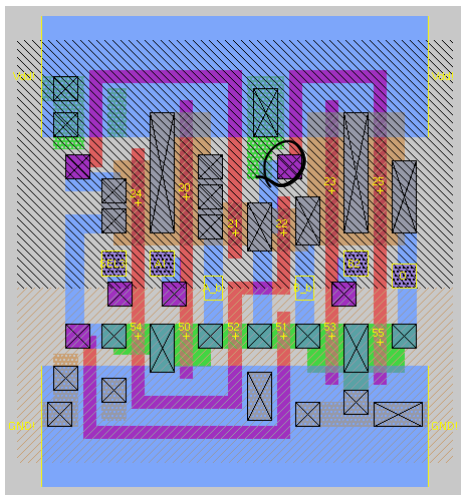


7.

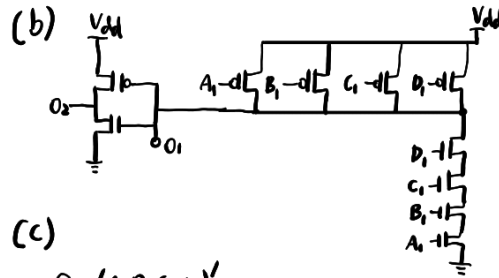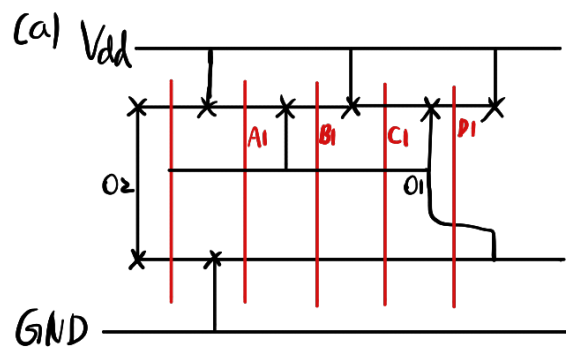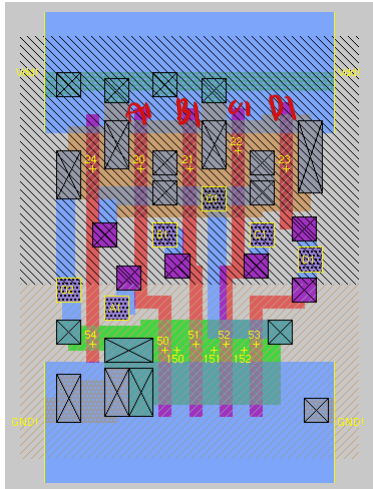




(c) $O_1 = (A_1 B_1 C_1 D_1)'$
 $O_2 = A_1 B_1 C_1 D_1$

8.

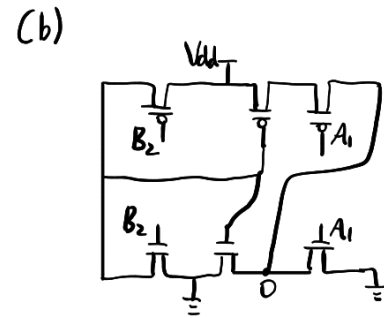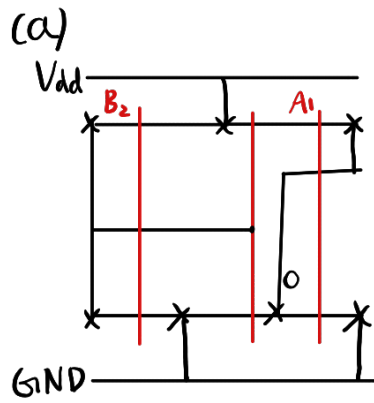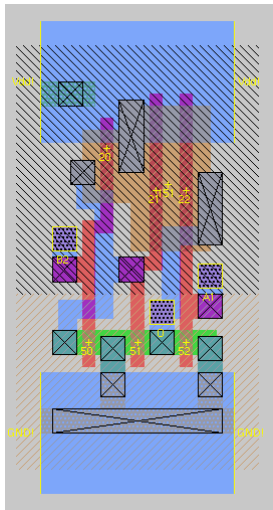




(c) $O = A_1' B_2$

9.

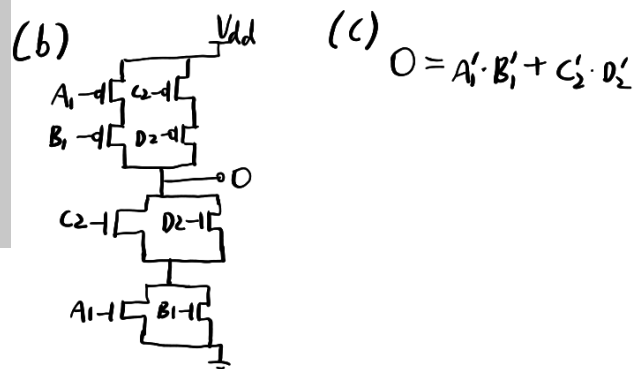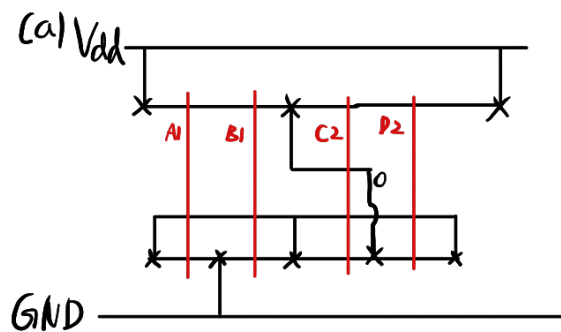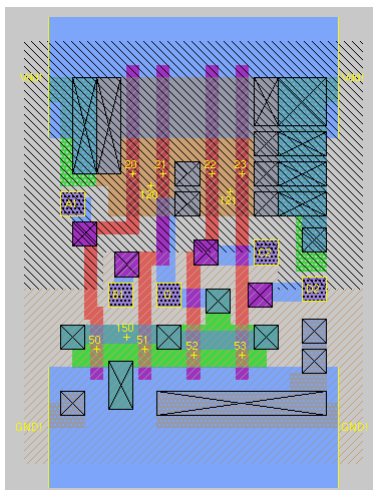

(c) $O = A_1' B_1' + C_2 D_2$

10.

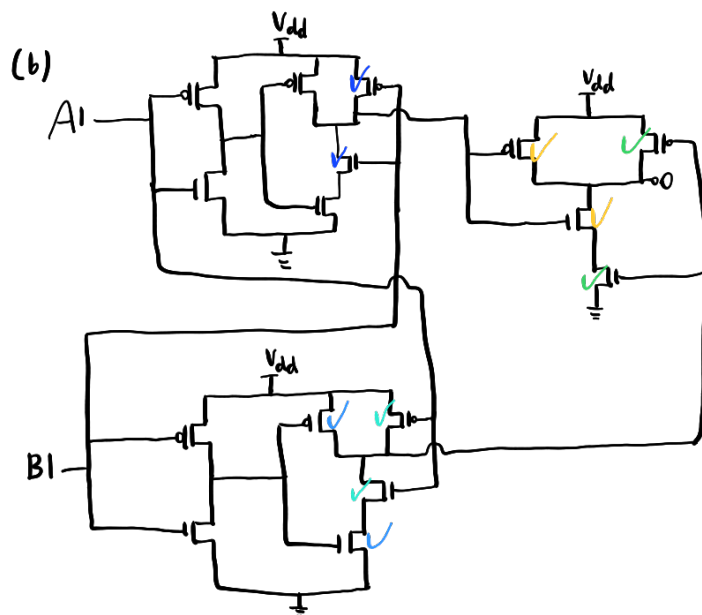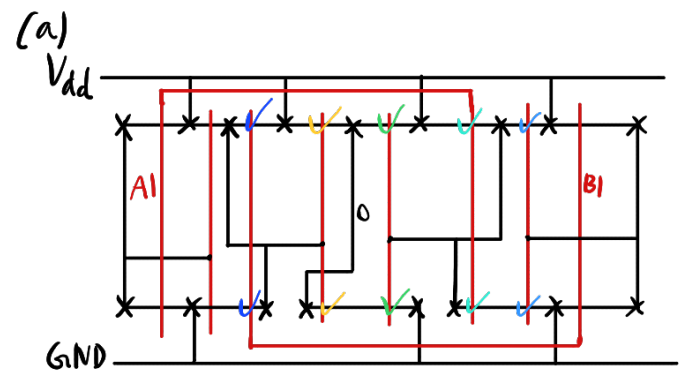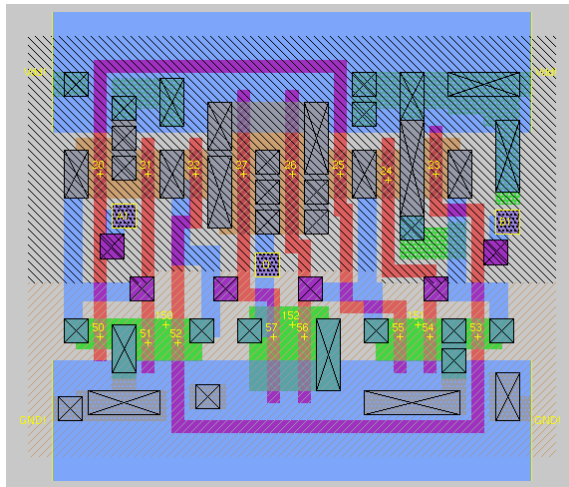

(c)

$$O = A_1' B_1 + A_1 B_1'$$

$$= A_1 \oplus B_1$$